
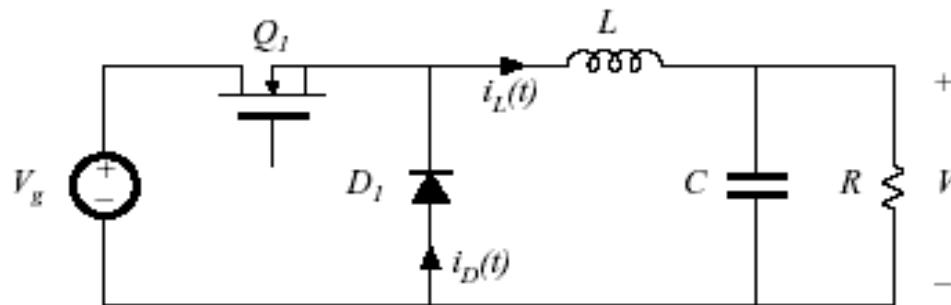


BUCK : CCM

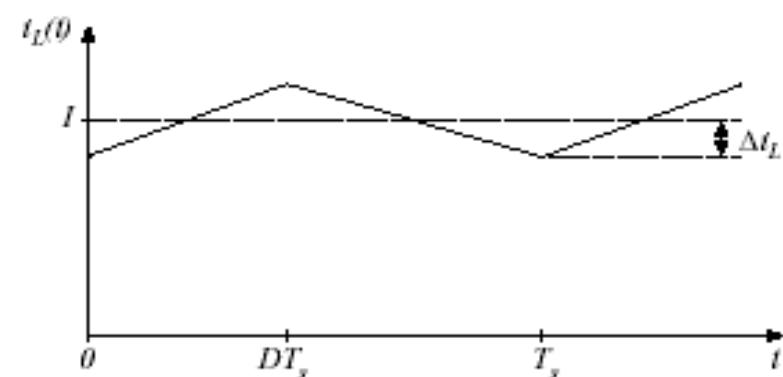
Buck converter example, with single-quadrant switches



continuous conduction mode (CCM)



conducting devices: Q_1 | D_1 | Q_1

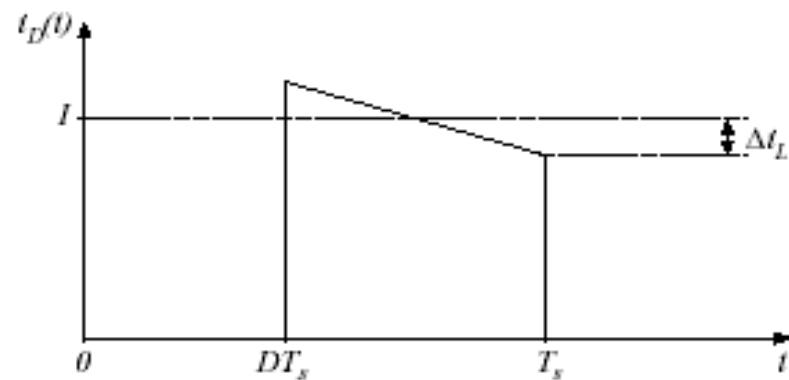

Minimum diode current is $(I - \Delta i_L)$

Dc component $I = V/R$


Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DDT_s}{2L}$$


Note that I depends on load, but Δi_L does not.

BUCK : CCM - DCM - Boundary

Increase R , until $I = \Delta i_L$

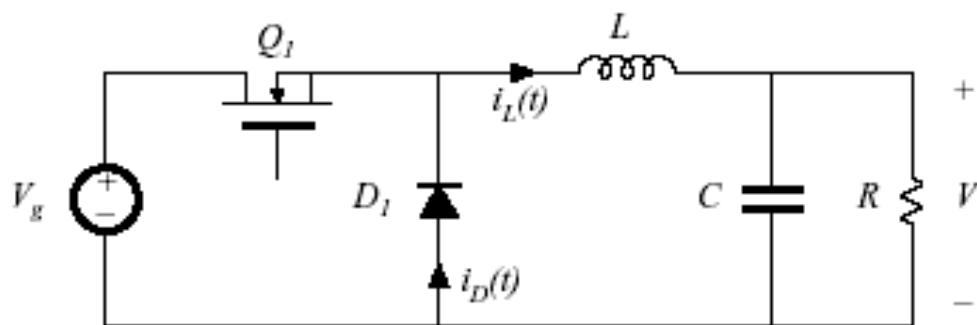

CCM-DCM boundary

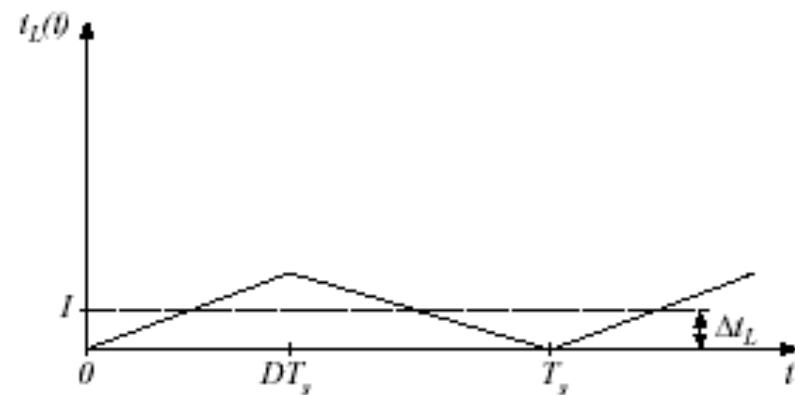


Minimum diode current is $(I - \Delta i_L)$

Dc component $I = V/R$

Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$

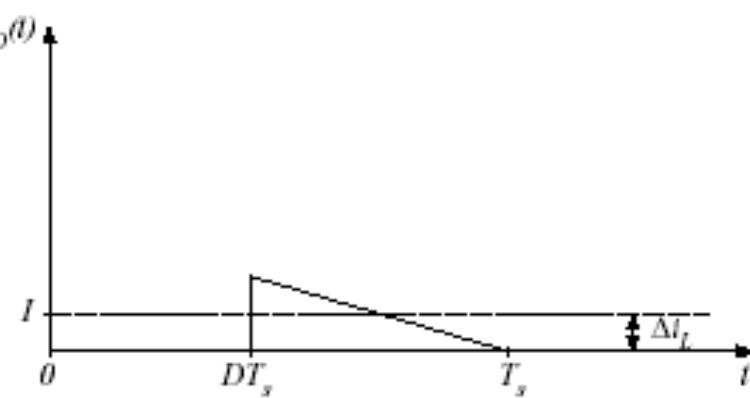
Note that I depends on load, but Δi_L does not.



BUCK : DCM

Increase R some more, such that $I < \Delta i_L$

Discontinuous conduction mode

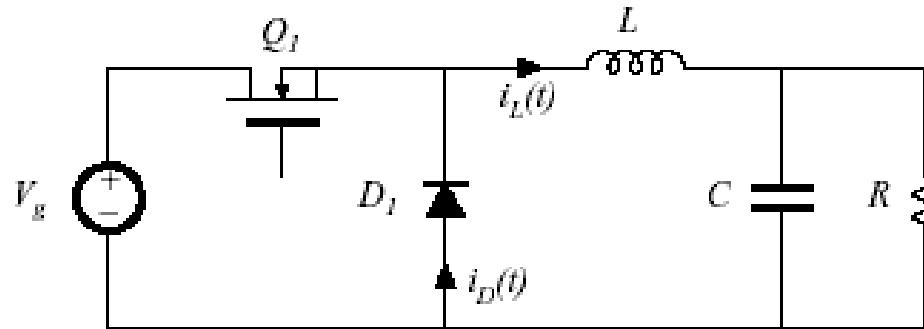

Minimum diode current is $(I - \Delta i_L)$



Dc component $I = V/R$

Current ripple is


$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD' T_s}{2L}$$

Note that I depends on load, but Δi_L does not.

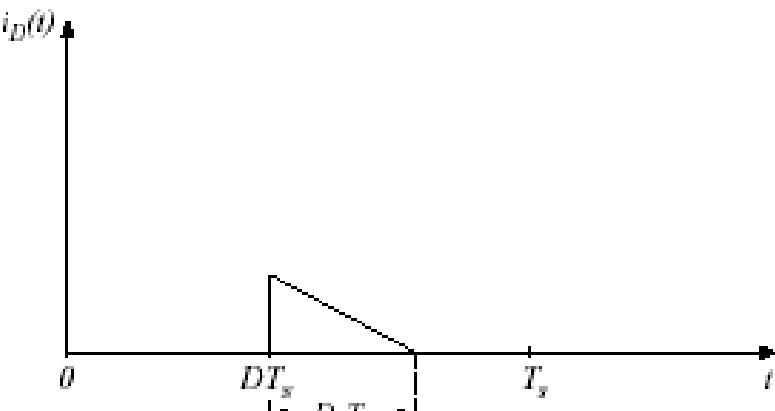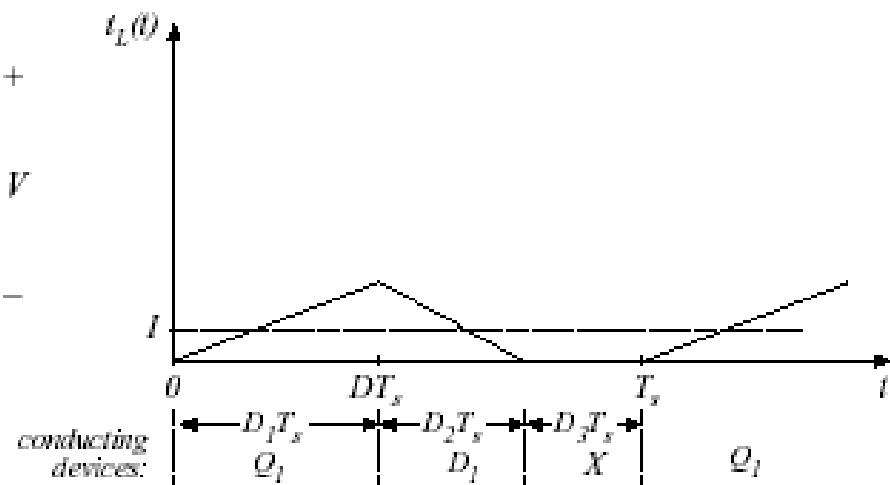The load current continues to be positive and non-zero.



BUCK : DCM

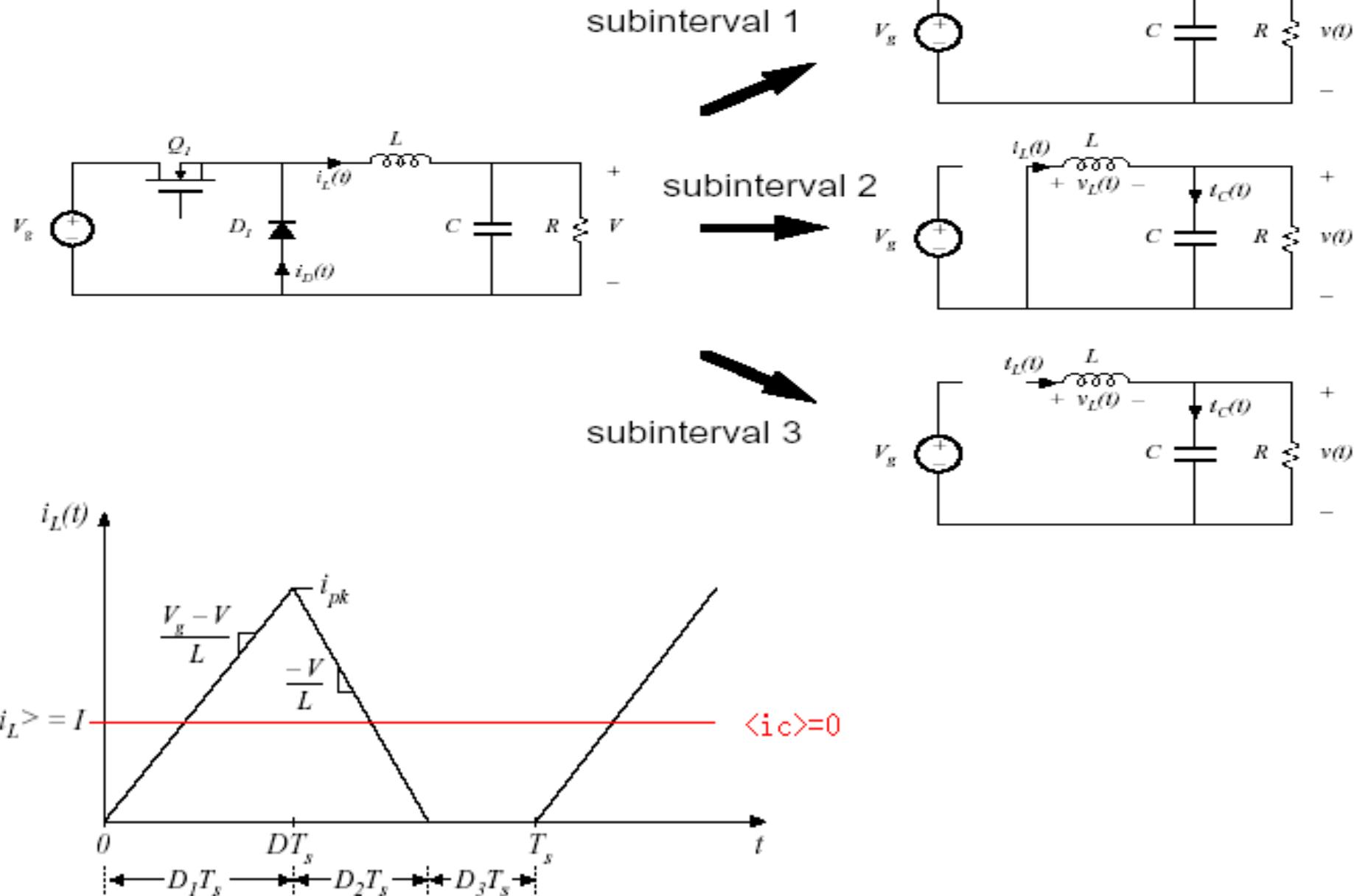

BOOST : DCM

