
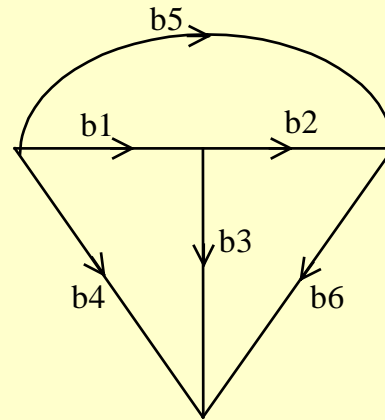


# CHAPTER 2 METHODS OF ANALYSIS

## 2-1 NETWORK TOPOLOGY

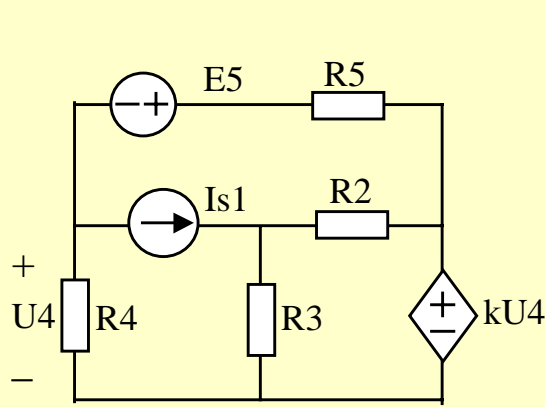

连通图

有向拓扑图

A given circuit and its linear graph (or simply a graph)

Node : A point at which two or more elements have a common connection.






Branch : A single path, containing one simple element, which connects one node to any other node.



Tree ( 树 ) : A set of branches which does not contain any loops and connects every node to every other nodes.

Cotree ( 余树 ) : After a tree has been specified, those branches that are not part of the tree form the cotree.

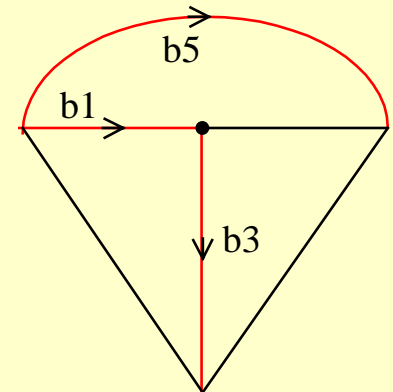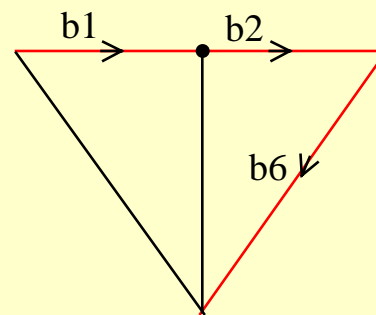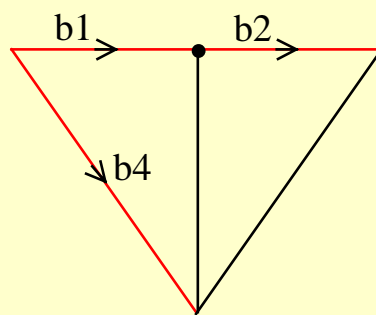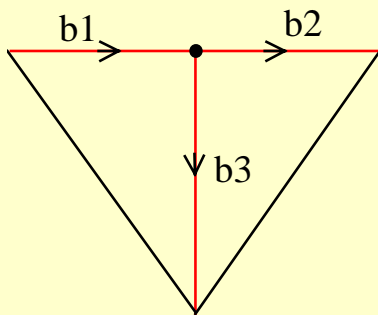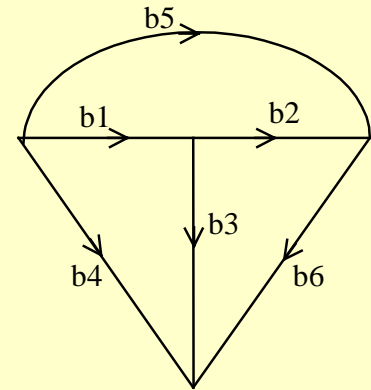Link ( 连支 ) : Any branch belonging to the cotree.






Check Your Understanding :

一个有 $n$ 个节点、 $b$ 条支路的连通图，连支数 $l$ 为？

$$l=b - (n - 1)$$

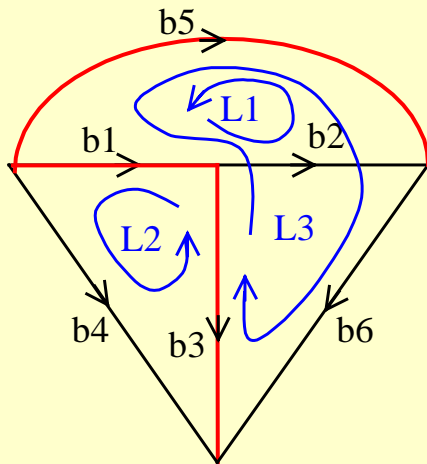基本回路（单连支回路）：该回路中只包含一条连支，其它都是树支。规定基本回路的方向与其中连支的方向一致。



$$L1 : U_{b1} + U_{b2} - U_{b5} = 0$$

$$L2 : - U_{b1} - U_{b3} + U_{b4} = 0$$

$$L3 : - U_{b1} - U_{b3} + U_{b5} + U_{b6} = 0$$



Mesh(网孔) : A loop which does not contain any other loops within it.

$$m1 : - U_{b1} - U_{b2} + U_{b5} = 0$$


$$m2 : U_{b1} + U_{b3} - U_{b4} = 0$$

$$m3 : U_{b2} + U_{b6} - U_{b3} = 0$$

$$L1 : U_{b1} + U_{b2} - U_{b5} = 0$$

$$L2 : - U_{b1} - U_{b3} + U_{b4} = 0$$
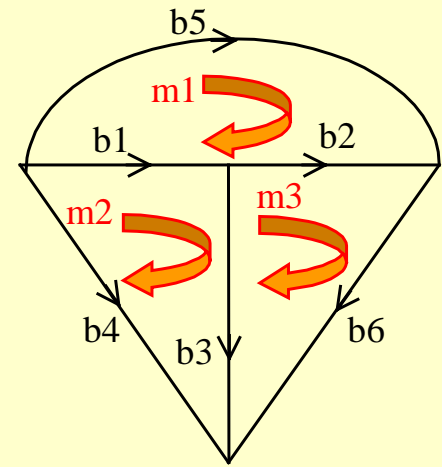
$$L3 : - U_{b1} - U_{b3} + U_{b5} + U_{b6} = 0$$



## 2-2 支路电流法 BRANCH ANALYSIS

以支路电流为未知量，直接应用KCL和KVL建立电路方程，从方程中解出各支路电流。

$$a . - I_1 + I_2 + I_4 = 0$$


$$b . - I_2 - I_3 - I_5 = 0$$

$$c . - I_4 + I_5 - I_6 = 0$$

$$d . I_1 + I_3 + I_6 = 0$$

独立节点数：全部节点数 - 1

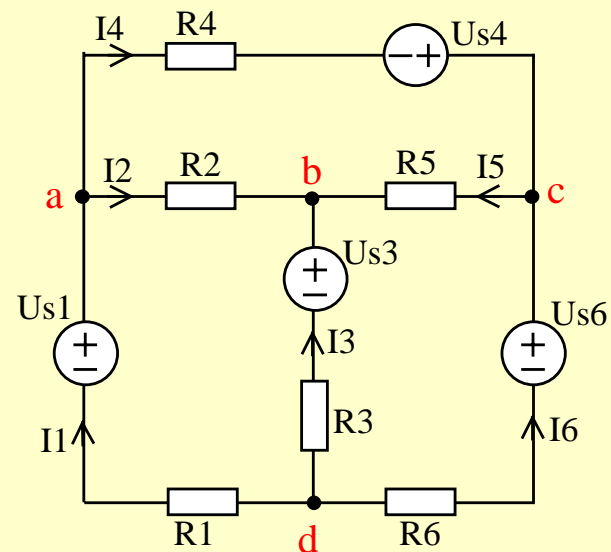
An independent node is a node whose voltage cannot be derived from the voltage of another node.



$$m1 : U_{S1} - U_{S3} = R_2 I_2 - R_3 I_3 + R_1 I_1 ;$$

$$m2 : U_{S4} = R_5 I_5 - R_2 I_2 + R_4 I_4 ;$$
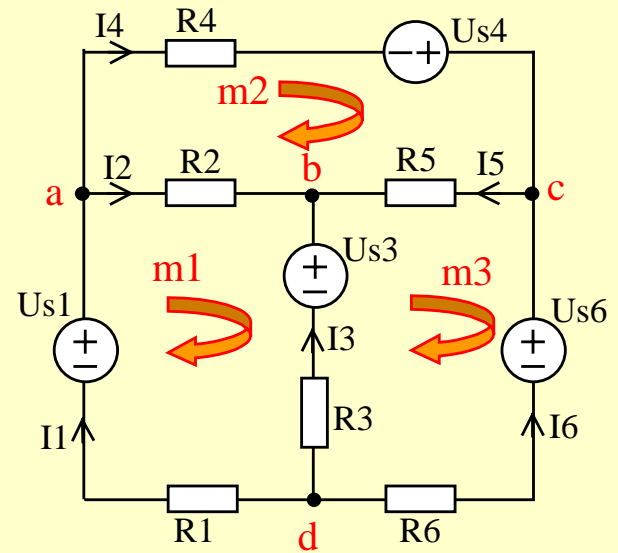
$$m3 : U_{S3} - U_{S6} = -R_5 I_5 - R_6 I_6 + R_3 I_3$$



例：  $R_1=1\Omega$  ,  $R_3=2\Omega$  ,  $U_{S1}=2V$  ,  $I_{S2}=0.5A$  , 求  $I_3$  ,  $P_U$  ,  $P_I$ 。

解：

$$a : I_1 + I_3 = I_{S2} \quad (1)$$

$$U_{ab} = R_1 I_1 - U_{S1} , U_{ab} = R_3 I_3$$

$$R_1 I_1 - U_{S1} = R_3 I_3$$


$$\text{回路电压方程： } U_{S1} = R_1 I_1 - R_3 I_3 \quad (2)$$

$$\Rightarrow I_1 = 1A , I_3 = -0.5A$$

$$\Rightarrow U_{ab} = R_3 I_3 = -1V$$

$$P_U = U_{S1} I_1 = 2W \text{ (发出功率) ,}$$
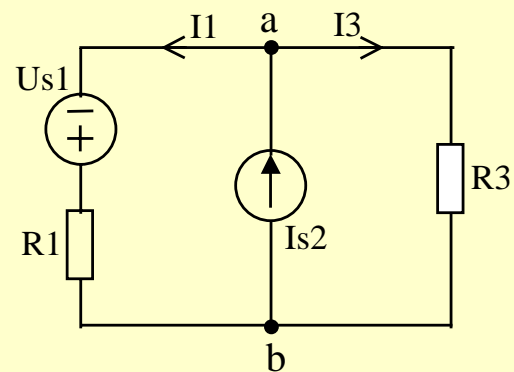
$$P_I = U_{ab} I_{S2} = -0.5W \text{ (吸收)}$$



例：  $R_2=2\Omega$  ,  $R_3=3\Omega$  ,  $U_{S3}=3V$  ,  $g_m=1S$  , 求  $I_2$  ,  $I_3$ 。

解：


$$a : g_m U_3 = I_2 + I_3 ,$$

$$U_3 = R_3 I_3 , \Rightarrow I_2 - 2I_3 = 0$$

$$\text{网孔电压方程： } U_{S3} = -R_2 I_2 + R_3 I_3 ,$$

$$\Rightarrow -2I_2 + 3I_3 = 3$$

$$\Rightarrow I_2 = -6A , I_3 = -3A$$

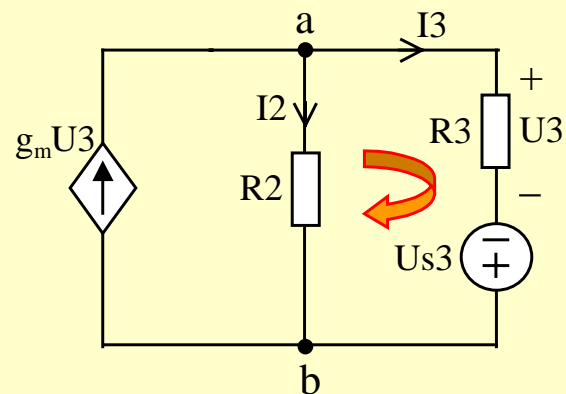



## 2-3 回路电流法 LOOP ANALYSIS

以基本回路电流为独立变量，在基本回路中建立KVL方程，解方程组得回路电流，随后确定支路电流。

基本回路电流：在基本回路（单连支回路）中，由连支电流形成的环流，简称回路电流。

Steps :

constructing a suitable tree ;

assigning a current reference to each link ;

KVL equations must be written around each of loops.



$$I1 : -U_{S1} + U_{S6} = R_1 I_1 + R_6 I_6 + R_5 I_5 + R_4 I_4$$

$$I_4 = I_1 + I_2 ,$$

$$I_5 = I_4 - I_3 = I_1 + I_2 - I_3 ,$$


$$I_6 = I_1 - I_3$$

$$I1 : (R_1 + R_4 + R_5 + R_6) I_1 + (R_4 + R_5) I_2 - (R_5 + R_6) I_3 = -U_{S1} + U_{S6}$$

$$I2 : (R_4 + R_5) I_1 + (R_4 + R_5) I_2 - R_5 I_3 = -U_{S2}$$

$$I3 : -(R_5 + R_6) I_1 - R_5 I_2 + (R_3 + R_5 + R_6) I_3 = -U_{S6}$$
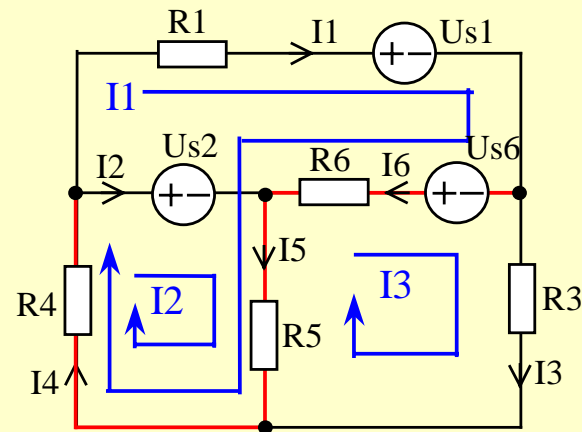
$$\text{即} : R_{11} I_1 + R_{12} I_2 + R_{13} I_3 = \sum_1 U_S$$



$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} \sum_1 U_s \\ \sum_2 U_s \\ \sum_3 U_s \end{bmatrix}$$

$R_{ij} (i=j)$  : 自电阻, Sum of the resistances in loop  $i$

$R_{ij} (i \neq j)$  : 互电阻, Sum of the resistances in common with loops  $i$  and  $j$ .

$\sum_1 U_s$  : Sum of all independent voltage sources in loop 1 , with voltage rise treated as positive.



例： $R_1=1\Omega$ ， $R_4=4\Omega$ ， $R_5=5\Omega$ ， $R_6=6\Omega$ ， $I_{S2}=2A$ ， $I_{S3}=3A$ ， $U_{S4}=4V$ ，求各支路电流。

解：

选456为树。

$$I_2 = I_{S2} = 2A, \quad I_3 = I_{S3} = 3A$$


$$I1 \text{回路} : (R_1 + R_4 + R_6)I_1 + R_4 I_2 - R_6 I_3 = U_{S4}$$

$$\Rightarrow I_1 = 14/11 = 1.27A,$$

$$I_4 = I_1 + I_2 = 36/11A,$$

$$I_5 = I_2 + I_3 = 5A,$$

$$I_6 = I_1 - I_3 = -19/11A。$$

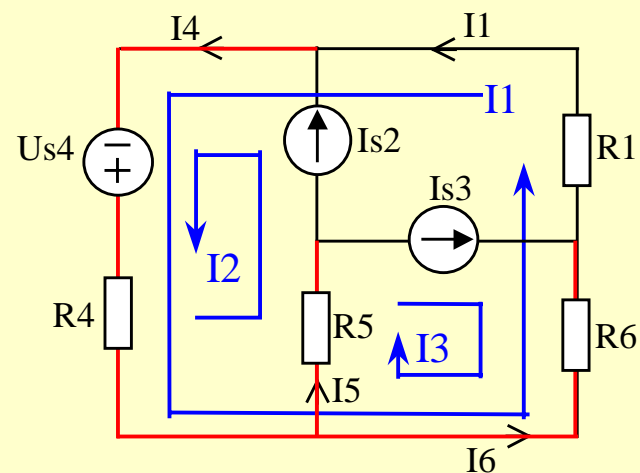

例： $R_1=1\Omega$ ， $R_2=2\Omega$ ， $R_3=3\Omega$ ， $R_4=4\Omega$ ， $I_{S5}=5A$ ，要使 $I_3=0$ ，求 $g_m$ 。

解：

选树如图。


$$I_4 \text{回路} : (R_1+R_2+R_3+R_4)I_4 + (R_1+R_2) g_m U_4 - (R_2+R_3)I_{S5} = 0$$

$$U_4 = R_4 I_4$$

$$I_4 = \frac{25}{10 + 12g_m}$$

$$I_3 = I_4 - I_{S5} = \frac{25}{10 + 12g_m} - 5 = 0$$

$$g_m = -\frac{5}{12} S$$

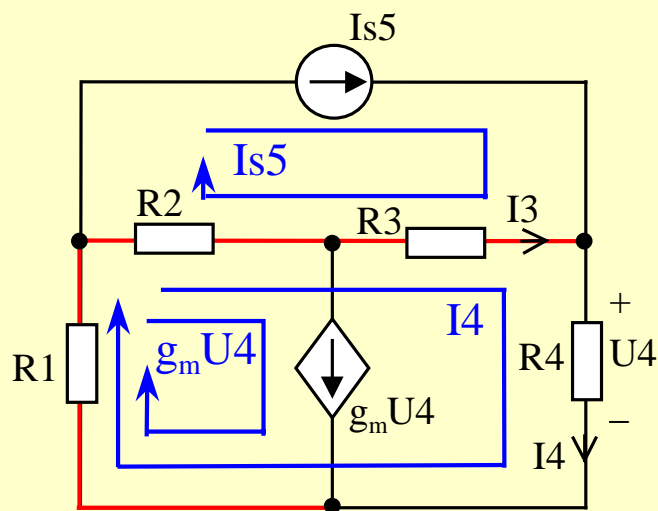

## 2-4 网孔电流法 MESH ANALYSIS

A loop is any closed path, and a mesh is a loop which does not contain any other loops within it.

A mesh current is a current that flows only around the perimeter of a mesh, may often be identified as a branch current.


$$I_{m1} : (R_1 + R_2 + R_3)I_{m1} - R_2I_{m2} - R_3I_{m3} = U_{S1} - U_{S3}$$

$$I_{m2} : -R_2I_{m1} + (R_2 + R_4 + R_5)I_{m2} - R_5I_{m3} = U_{S4}$$

$$I_{m3} : -R_3I_{m1} - R_5I_{m2} + (R_3 + R_5 + R_6)I_{m3} = U_{S3} - U_{S6}$$

$$I_1 = I_{m1} \quad , \quad I_2 = I_{m1} - I_{m2} \quad , \quad I_3 = -I_{m1} + I_{m3} \quad ,$$
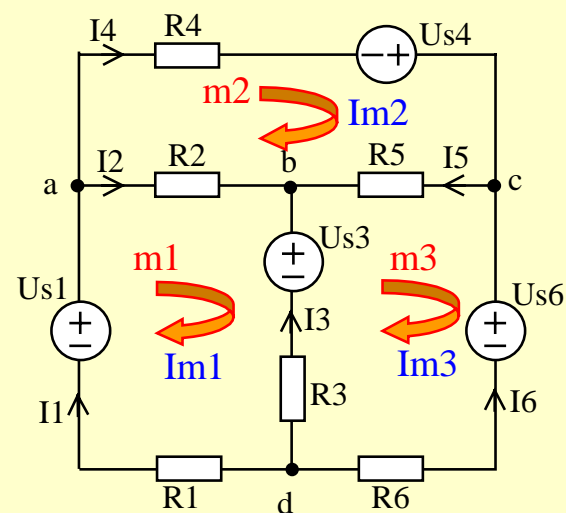
$$I_4 = I_{m2} \quad , \quad I_5 = I_{m2} - I_{m3} \quad , \quad I_6 = -I_{m3}$$



例： $E_1=1V$ ， $E_3=6V$ ， $I_S=6A$ ， $R_1=3\Omega$ ， $R_2=2\Omega$ ， $R_3=1\Omega$ ， $R_4=4\Omega$ ，  
求网孔电流。

解：

$$I_{m3}=I_S=6A$$

$I_{m1}$ 网孔：


$$(R_1+R_2)I_{m1}-R_2I_{m2}=E_1$$

$I_{m2}$ 网孔：

$$-R_2I_{m1}+(R_2+R_3+R_4)I_{m2}-R_3I_{m3}=E_3$$

$$\text{即：} 5I_{m1}-2I_{m2}=1, \quad -2I_{m1}+7I_{m2}-1 \times 6=6$$
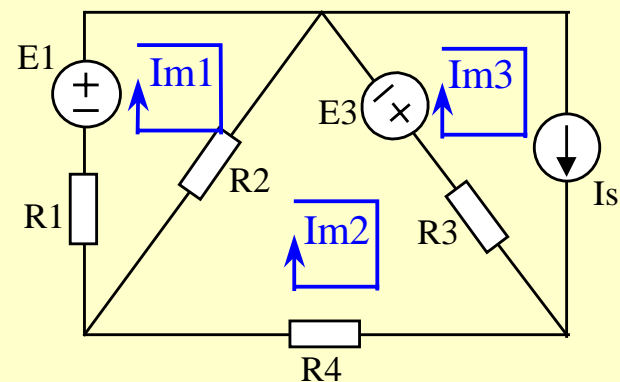
$$\Rightarrow I_{m1}=1A, \quad I_{m2}=2A。$$



例：  $R_S=R_1=1\Omega$  ,  $R_2=2\Omega$  ,  $R_3=3\Omega$  ,  $\mu=3$  , 要使  $I_3=3A$  , 确定  $U_{S1}$ 。

解：

Im1网孔：

$$(R_1+R_2+R_S)I_{m1}-R_2I_{m2}=U_{S1}-\mu U$$

Im2网孔：

$$-R_2I_{m1}+(R_2+R_3)I_{m2}=\mu U$$

$$U=U_{S1}-R_S I_{m1} ,$$


代入上两式，得：

$$[(1-\mu)R_S+R_1+R_2]I_{m1}-R_2I_{m2}=(1-\mu)U_{S1} ;$$

$$(\mu R_S - R_2)I_{m1}+(R_2+R_3)I_{m2}=\mu U_{S1}$$

$$\Rightarrow 7I_{m2}=5U_{S1}$$
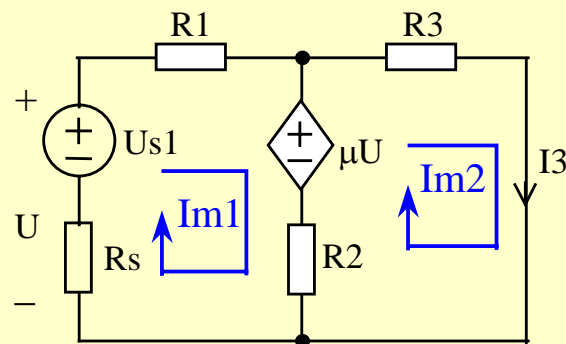
$$\text{令： } I_3=I_{m2}=3A , \Rightarrow U_{S1}=4.2V$$







# Check Your Understanding : Calculate the mesh currents.

$$I_{m1} : I_{m1} = I_{S5}$$

$$I_{m2} : -R_2 I_{m1} + (R_1 + R_2) I_{m2} = 0$$



$$R_1 I_1 + R_2 I_2 + U_{gU4} = 0 \quad U_{gU4} = R_3 I_3 + R_4 I_4$$



A supermesh results when two meshes have a dependent or independent current source in common.

$$R_1 I_1 + R_2 I_2 + R_3 I_3 + R_4 I_4 = 0, \quad I_2 = I_1 - I_{S5}, \quad I_3 = I_4 - I_{S5}$$

$$I_1 = g_m U_4 + I_4$$

$$U_4 = R_4 I_4$$

$$I_1 = I_{m2}, \quad I_4 = I_{m3}$$

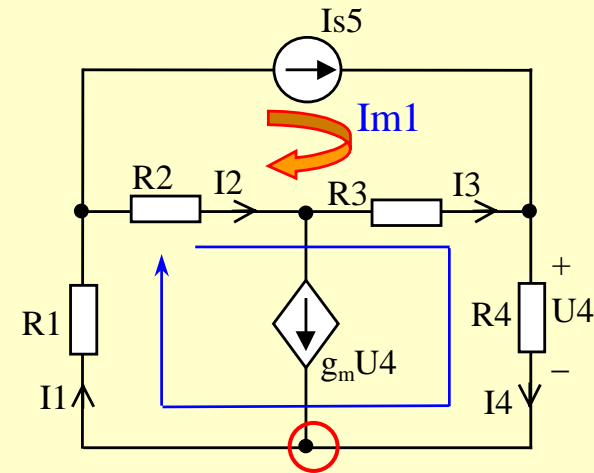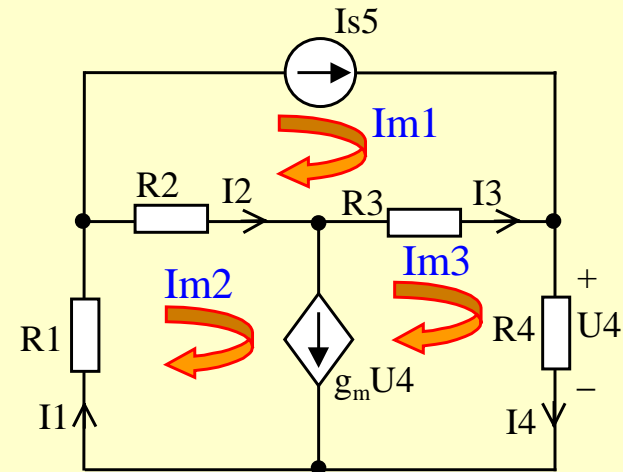

## 2-5 节点电压法

### NODE-VOLTAGE ANALYSIS / NODAL ANALYSIS

#### 一、Steps :

Select a node as the reference node.

Apply KCL to each of the  $n-1$  nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.

Solve the resulting simultaneous equations to obtain the unknown node voltages.



Node 1 :

$$-I_1 - I_{S2} - I_3 + I_{S4} + I_5 + I_6 = 0$$

$$I_1 = G_1(U - U + U_{S1}) ,$$

$$I_3 = G_3(U - U ) ,$$


$$I_5 = G_5(U - U ) ,$$

$$I_6 = G_6(U - U + U_{S6})$$

$$G_6 = \frac{1}{R'_6 + R''_6} = \frac{G'_6 G''_6}{G'_6 + G''_6}$$

$$(G_1 + G_3 + G_5 + G_6)U - G_1 U - G_3 U - (G_5 + G_6)U = G_1 U_{S1} - G_6 U_{S6} + I_{S2} - I_{S4}$$
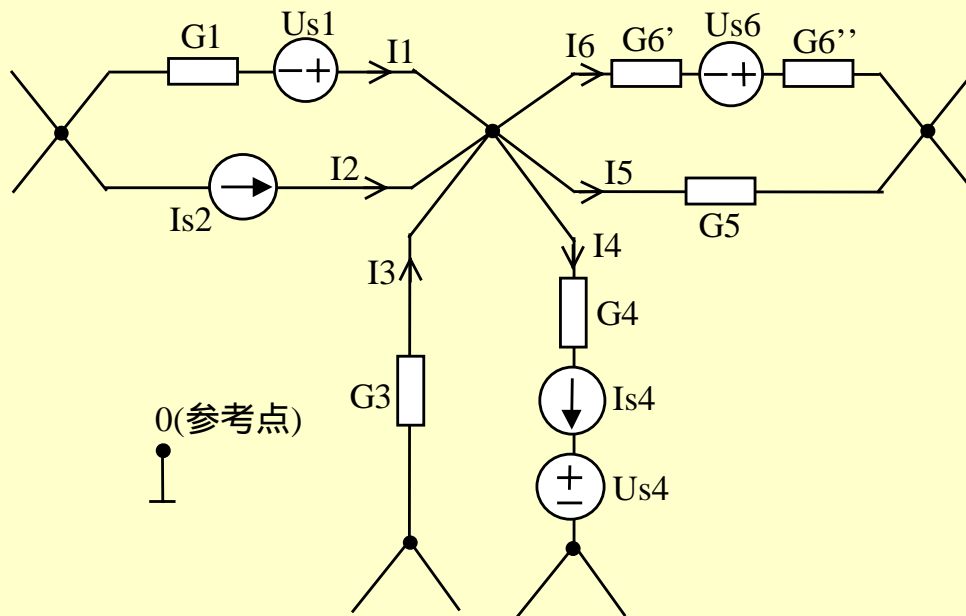
$$G_{11}U + G_{12}U + G_{13}U + G_{15}U = \sum_{(1)} GU_s + \sum_{(1)} I_s$$



$$G_{11}U + G_{12}U + G_{13}U + G_{15}U = \sum_{(1)} GU_s + \sum_{(1)} I_s$$


$G_{ij}$  (  $i=j$  ) : 自电导 , Sum of the conductances connected to node  $i$  .

$G_{ij}$  (  $i \neq j$  ) : 互电导 , Negative of the sum of the conductances directly connecting nodes  $i$  and  $j$  .

( Turn OFF all sources. )

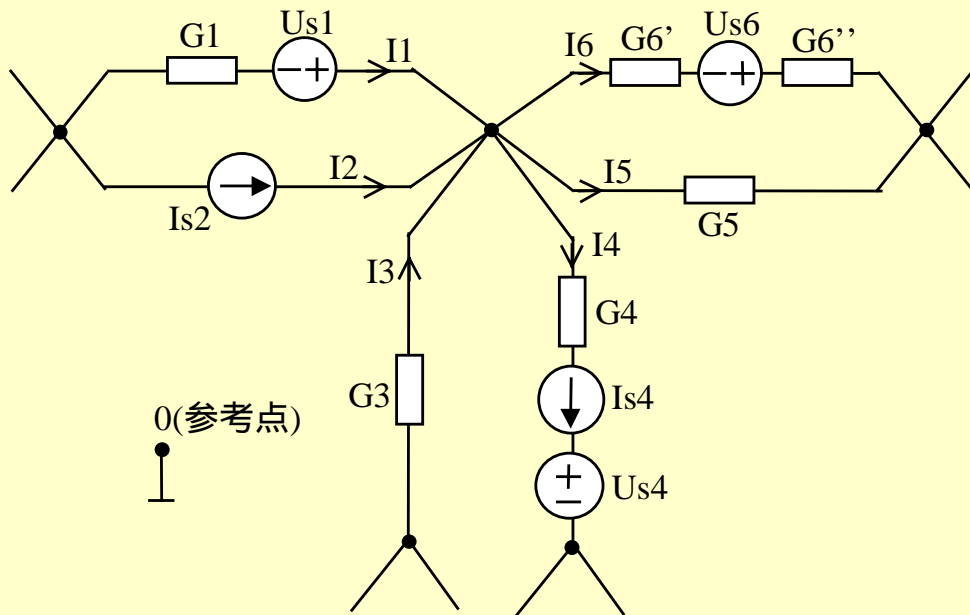$\sum_{(1)} GU_s + \sum_{(1)} I_s$  : Sum of all sources directly connected to node 1, with currents entering the node treated as positive.





$$G_6 = \frac{1}{R'_6 + R''_6} = \frac{G'_6 G''_6}{G'_6 + G''_6}$$

$$(G_1 + G_3 + G_4 + G_5 + G_6)U - G_1 U - G_3 U - G_4 U - (G_5 + G_6)U$$

$$= G_1 U_{S1} - G_6 U_{S6} + I_{S2} - I_{S4} + G_4 U_{S4}$$




$$(G_1 + G_3 + G_5 + G_6)U - G_1 U - G_3 U - (G_5 + G_6)U = G_1 U_{S1} - G_6 U_{S6} + I_{S2} - I_{S4}$$

$$(G_1 + G_3 + \mathbf{G_4} + G_5 + G_6)U - G_1 U - G_3 U - \mathbf{G_4 U} - (G_5 + G_6)U = G_1 U_{S1} - G_6 U_{S6} + I_{S2} - I_{S4} + \mathbf{G_4 U_{S4}}$$

**Turn OFF all sources !!! 电源置零**



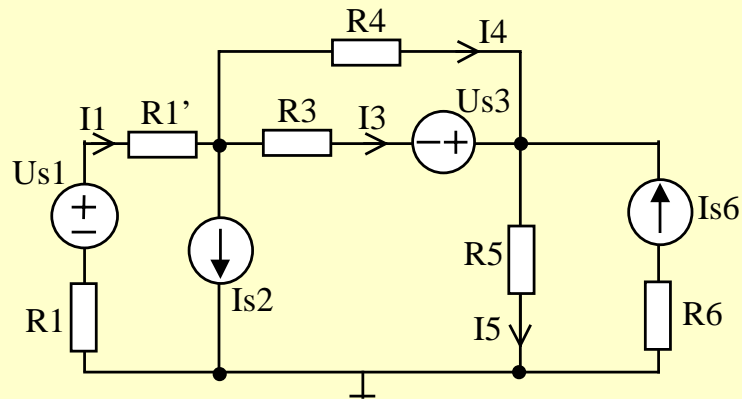例：  $R_1=R_1'=0.5\Omega$  ,  
 $R_3=R_4=R_5=R_6=1\Omega$  ,  $U_{S1}=1V$  ,  
 $U_{S3}=3V$  ,  $I_{S2}=2A$  ,  $I_{S6}=6A$  ,  
 求各支路电流。



解：取节点 为参考节点：

节点 ：

$$\left(\frac{1}{R_1+R_1'} + \frac{1}{R_3} + \frac{1}{R_4}\right)U_{(1)} - \left(\frac{1}{R_3} + \frac{1}{R_4}\right)U_{(2)} = \frac{U_{S1}}{R_1+R_1'} - \frac{U_{S3}}{R_3} - I_{S2}$$

节点 ：

$$-\left(\frac{1}{R_3} + \frac{1}{R_4}\right)U_{(1)} + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)U_{(2)} = \frac{U_{S3}}{R_3} + I_{S6}$$


$$\Rightarrow U_{(1)} = 1.2V , U_{(2)} = 3.8V。$$

$$I_1 = (U_{S1} - U_{(1)}) / (R_1 + R_1') = -0.2A , I_3 = (U_{(1)} - U_{(2)} + U_{S3}) / R_3 = 0.4A$$

$$I_4 = (U_{(1)} - U_{(2)}) / R_4 = -2.6A , I_5 = U_{(2)} / R_5 = 3.8A$$



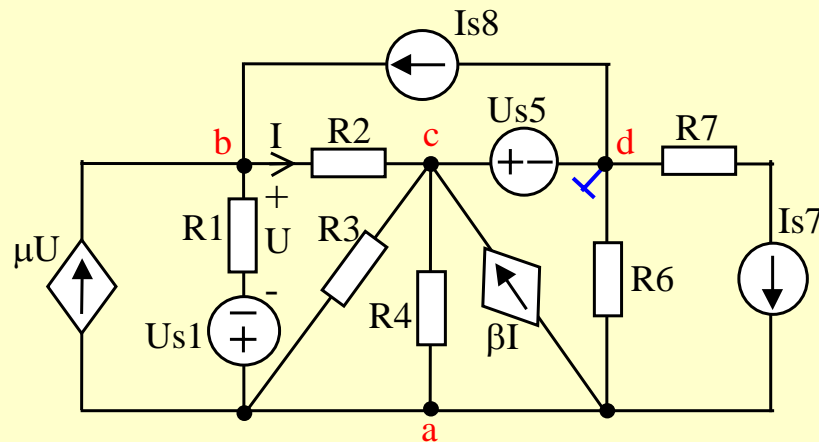例：  $R_1=R_2=R_3=R_4=R_6=2\Omega$  ,  
 $R_7=6\Omega$  ,  $U_{S1}=4V$  ,  $U_{S5}=10V$  ,  
 $I_{S7}=1A$  ,  $I_{S8}=4A$  ,  $\mu=2$  ,  
 $\beta=2$  , 求各节点电压。



解：选d为参考节点，  $U_c=10V$

$$a : (G_1+G_3+G_4+G_6)U_a - G_1U_b - (G_3+G_4)U_c = G_1U_{S1} - \mu U - \beta I + I_{S7}$$

$$b : -G_1U_a + (G_1+G_2)U_b - G_2U_c = \mu U - G_1U_{S1} + I_{S8}$$

$$\left(\frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2}\right)U_a - \frac{1}{2}U_b - \left(\frac{1}{2} + \frac{1}{2}\right)U_c = \frac{1}{2} \times 4 - 2U - 2I + 1$$

$$-\frac{1}{2}U_a + \left(\frac{1}{2} + \frac{1}{2}\right)U_b - \frac{1}{2}U_c = -\frac{1}{2} \times 4 + 2U + 4$$

$$U = U_b - U_a + 4 ; \quad \Rightarrow U_b = 10V$$

$$I = 0.5 \times (U_b - U_c) = 0.5 \times (U_b - 10) \quad \Rightarrow U_a = 14V$$



## 二、改进节点法 MODIFIED NODAL ANALYSIS

$U_{S2}$  : 无伴电压源


Assign an unknown current to the branch which contains the voltage source.

$$a : U_a = U_{S1}$$

$$b : -G_3 U_a + (G_3 + G_5) U_b = -I_{S2}$$

$$c : -G_4 U_a + (G_4 + G_6) U_c = I_{S2}$$

$$U_b - U_c = U_{S2}$$

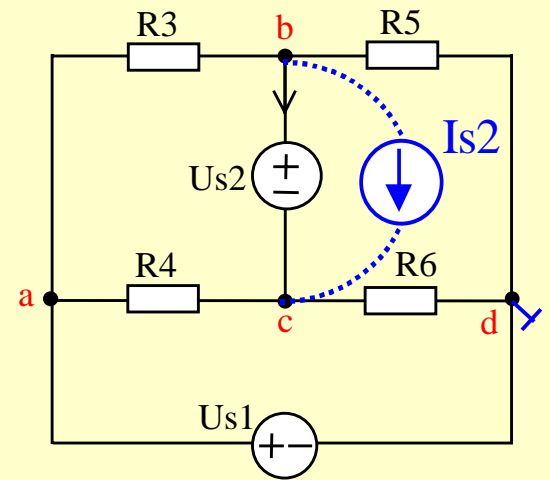



The other method is to treat node b, node c and the voltage source together as a sort of supernode and apply KCL to both nodes at the same time.


A supernode may be regarded as a closed surface enclosing the voltage source and its two nodes.

$$a : U_a = U_{s1} \quad (1)$$

$$b \& c : I_3 + I_4 = I_5 + I_6$$

$$\frac{U_a - U_b}{R_3} + \frac{U_a - U_c}{R_4} = \frac{U_b}{R_5} + \frac{U_c}{R_6} \quad (2)$$

$$U_b - U_c = U_{s2} \quad (3)$$

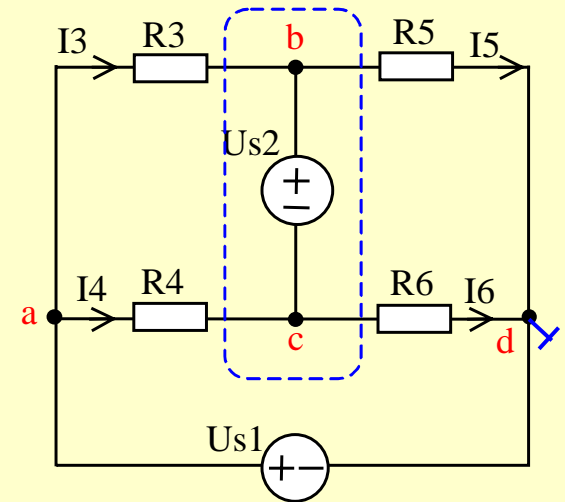

## SUMMARY

Which method is the best or most efficient? The choice is dictated by two factors.

The first factor is the nature of the particular network. The key is to select the method that results in the smallest number of equations.

The second factor is the information required.

By the way, nodal analysis is more amenable to solution by computer, as it is easy to program.

